

# Correction

(1)

Exercise 1:  $U = 240V$ .

M1:  $N=3$ :  $P_{M1} = 2kW$ ;  $\eta = 0.18$ ;  $\cos\phi_1 = 0.707$

M2:  $N=1$ :  $P_{M2} = 4kW$ ;  $\eta = 0.75$ ;  $\cos\phi_2 = 0.18$

1 Four  $P_3 = 8kW$

10/  $P_1$ ?  $P_1 = U \cdot I_1 \cdot \cos\phi_1 = \frac{P_{M1}}{\eta_1} = \frac{2}{0.18}$

$P_1 = 2.5 kW$

20/  $P_2$ ?  $P_2 = U \cdot I_2 \cdot \cos\phi_2 = \frac{P_{M2}}{\eta_2} = \frac{4}{0.75}$

$P_2 = 5.33 kW$

30/  $Q_1$ ?  $Q_1 = P_1 \times \tan\phi_1$   $\phi_1 = \cos^{-1}(0.707)$

$Q_1 = 2.5 \times \tan(\cos^{-1}(0.707)) = 2.5 kVar$

$Q_1 = 2.5 kVar$

40/  $Q_2$ ?  $Q_2 = P_2 \times \tan\phi_2$   $\phi_2 = \cos^{-1}(0.18)$

$Q_2 = 5.33 \times \tan(\cos^{-1}(0.18)) = 4 kVar$

$Q_2 = 4 kVar$

50/  $P_t$ ?  $Q_t$ ?

$Q_t = 3 P_1 + P_2 = P_F = 3 \times 2.5 + 5.33 + 8$

$P_t = 20.83 kW$

$Q_t = 3 Q_1 + Q_2 + \underbrace{Q_F}_0 = 3 \times 2.5 + 4 + 0$

$Q_t = 11.5 kVar$

6°) Notem 1:

$$I_1 = \frac{P_1}{U \times \cos \varphi_1} = \frac{2500}{240 \times 0,707} = 14,73 \text{ A}$$

$$\boxed{I_1 = 14,73 \text{ A}}$$

Notem 2:

$$I_2 = \frac{P_2}{U \times \cos \varphi_2} = \frac{5333}{240 \times 0,18} = 27,8 \text{ A}$$

$$\boxed{I_2 = 27,8 \text{ A}}$$

Four:

$$I_3 = \frac{P_3}{U \cos \varphi_3} = \frac{8000}{240 \times 1} = 33,33 \text{ A}$$

$$\boxed{I_3 = 33,33 \text{ A}}$$

7°)  $I_t$ ?

e) méthode Boucherot

$$\underline{I}_t = \frac{S}{U}, \quad S = \sqrt{P_t^2 + Q_t^2}$$

$$S = \sqrt{20183^2 + 11,5^2} = 23,8 \text{ kVA}$$

$$\underline{I}_t = \frac{23,8 \times 10^3}{240} = 99 \text{ A}$$

$$\boxed{I_t = 99 \text{ A}}$$

b) Méthode de nombres complexes

$$\underline{I}_t = 3\underline{I}_1 + \underline{I}_2 + \underline{I}_3$$

$$\varphi_1 = \cos^{-1}(0,707) = \pi/4$$

avec  $\underline{I}_1 = [14,73 j - \pi]$

$$\underline{I}_1 = 14,73 \cos(-\pi/4) + j 14,73 \cdot \sin(-\pi/4)$$



$$\underline{I}_1 = 1014 - j1014$$

(3)

$$\underline{I}_2 = [278; -0.1646]$$

$$\varphi_2 = \cos^{-1}(0.18) = 0.1646 \text{ rad}$$

les moteurs sont de nature inductive donc le courant i est en retard par rapport à la tension d'où le signe (-)

$$\underline{I}_3 = [33.33; 0] \quad \varphi_3 = \cos^{-1}(1) = 0$$

$$\underline{I}_2 = 278(\cos(-0.1646) + j\sin(-0.1646)) = 278(0.985 - j0.1646)$$

$$\underline{I}_t = 3\underline{I}_1 + \underline{I}_2 + \underline{I}_3 = 3 \times (1014 - j1014) + 221.24 - j16.7 + 33.33$$

$$\underline{I}_t = 86.77 - j47.9$$

valeur efficace de toute l'installation

$$I_t = \sqrt{86.77^2 + (-47.9)^2} = 99 \text{ mA}$$

$$\underline{I}_t = 99 \text{ mA}$$

99% facteur de puissance

$$k = \frac{P_t}{S} = \frac{20.83}{23.18} = 0.9025$$

autre méthode

$$\left( \begin{array}{l} \text{si } z = a + jb = [r, \theta] \\ \cos \theta = \frac{a}{r}, \sin \theta = \frac{b}{r} \end{array} \right)$$

$$\underline{I}_t = 86.77 - j47.9$$

$$\text{facteur de puissance } k = \frac{86.77}{99} = 0.875$$

$$110/ \quad k = 0,825$$

nouveau facteur de puissance  $k' = 0,96$

$Q_c$ ?  $\varphi' = \cos^{-1}(0,96) = 0,284 \text{ rad}$   
on calcule la nouvelle puissance réactive  $Q'$ :

$$Q' = Q_c + Q_b \Rightarrow Q_c = Q' - Q_b$$

$$Q' = P_t \times \tan \varphi' = 20,83 \times \tan(0,284)$$

$$\boxed{Q' = 6 \text{ kVAR}}$$

$$\text{donc } Q_c = Q' - Q_b = 6 - 11,5 = -5,5 \text{ kVAR}$$

$$\boxed{Q_c = -5,5 \text{ kVAR}}$$

- Comme  $Q_c = -U^2 C \omega \Rightarrow \boxed{C = \frac{-Q_c}{U^2 \omega}}$

$$\text{AN: } C = \frac{-(-5500)}{240^2 \times 314} = 0,000304 \text{ F}$$

$$\boxed{C = 304 \mu\text{F}}$$

$$110/ \quad I' = \frac{P_t}{U \times \cos \varphi'} = \frac{20,83 \times 10^3}{240 \times 0,96}$$

$$\boxed{I' = 90,4 \text{ A}}$$